

- HW4 posted - tentative ; due date to be determined
- Circuit kit will be handed out on Monday.  
We will start work on Circuit 1.

## Ch. 4 (partly already covered)

Conversion of English sentences to Boolean equations (and circuits)

### Example

"The alarm will ring if and only if (iff) the alarm switch is turned on and the door is not closed, or it is after 6pm and the door is not closed."

First step: match phrases with (propositional) variables, or literal

The alarm will ring iff the alarm switch is on and

the door is not closed or it is after 6pm and

the window is not closed.

Each phrase is true when the corresponding variable/literal is true; each phrase is false when the corresponding variable/literal is false

Note that we represent "the door is closed" with B and therefore "the door is not closed" as B'. Similarly for D.

Second step: write the expression for the variable corresponding to the desired output (here: Z, "the alarm will ring") using the other variables

$$Z = AB' + CD'$$

Third step: simplify according to De Morgan's laws or Boolean algebra

Here, the expression  $Z = AB' + CD'$  is already in sum-of-product form. It also has the minimum number of products and, among expressions with the minimum number of products, each product has the minimum size.

Q6  $Z =$  Elevator door opens


$S =$  Elevator is Stopped

$F =$  Elevator is level with Floor


$T =$  Timer has expired

$B =$  Button is pressed


$$Z = SFT' + SFB (= SF(T+B))$$

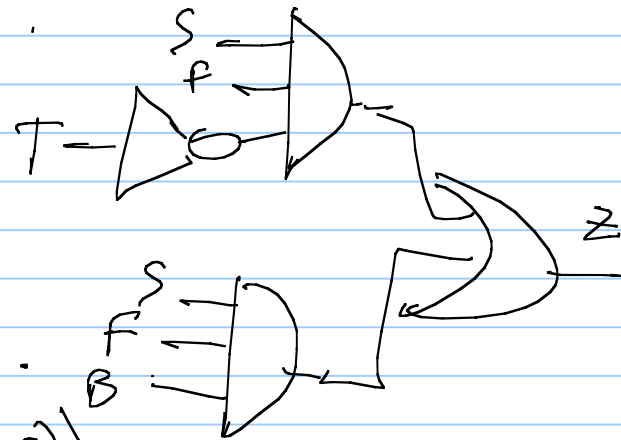


Circuit equivalent to the expression  $Z = AB' + CD'$ .

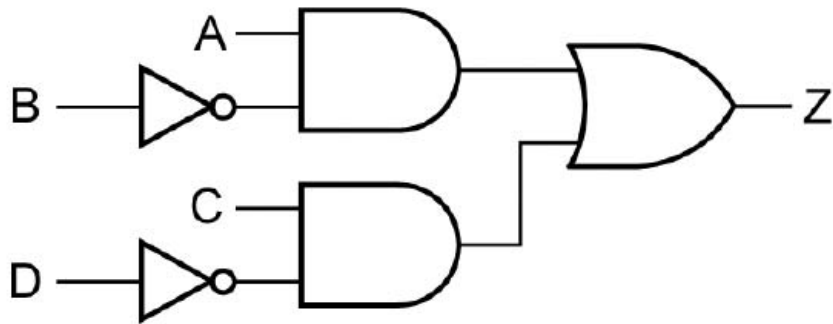

Section 4.1, p. 85

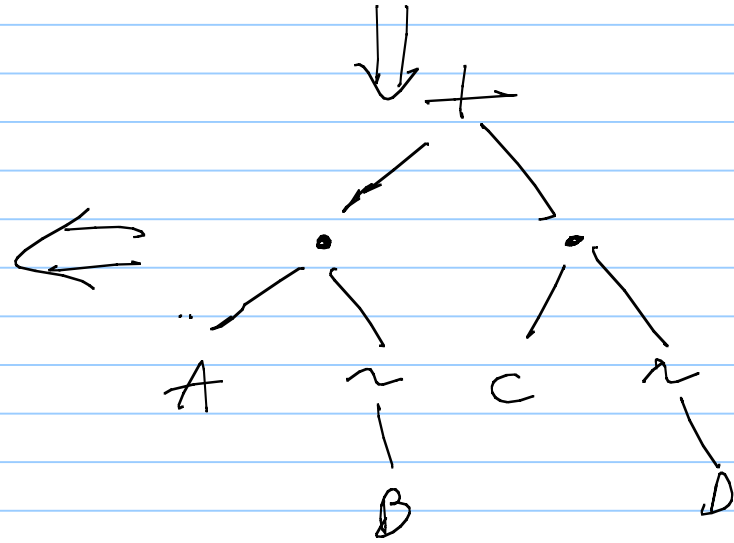
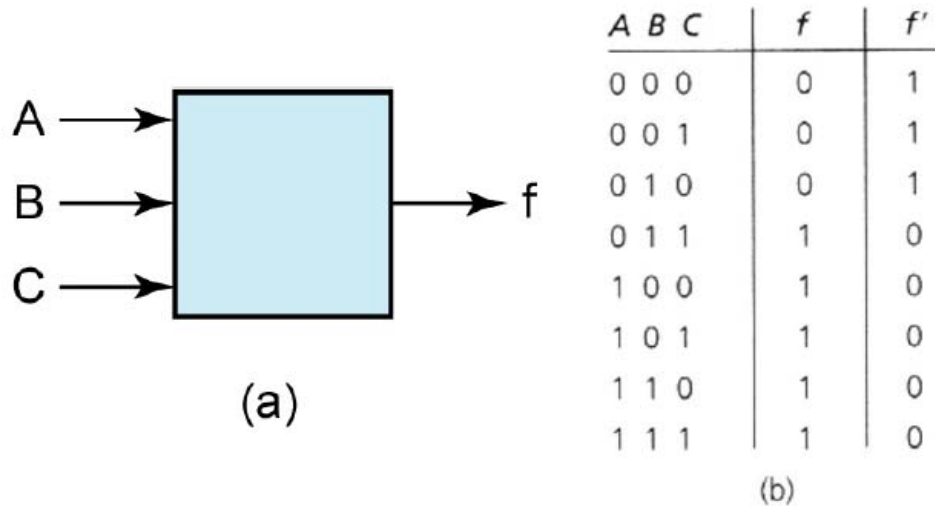
# Combinatorial design using a truth table (section 4.2)



$$\begin{aligned}
 f &= A'B'C + AB'C' + AB'C + ABC' + ABC \\
 &= A'B'C + AB' + AB = A'B'C + A \\
 &= [11D] = A + BC
 \end{aligned}$$

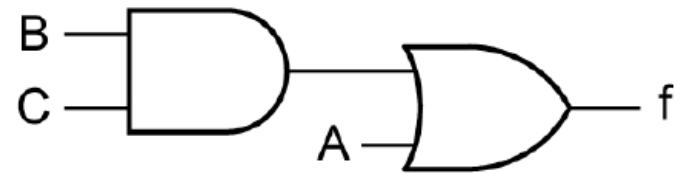


Figure 4-1: Combinational Circuit with Truth Table

$$\begin{aligned}
 f &= (A+B+c)(A+B+C')(A+B'+c) = \\
 &= [9D] = (A+B)(A+B'+c) = [8D], \text{ 2nd} \\
 &\text{distributive law} = A + B(B'+c) = A + BC
 \end{aligned}$$

$$f' = A'B'C' + A'B'C + A'BC'$$

$$f = (A'B'C' + A'B'C + A'BC')' = (A+B+C)(A+B+C')(A+B'+C)$$

$$= A'B' + A'BC' = A'(B' + Bc') = [11D] = A'(B'+C)$$

$$f = (A'(B'+C))' = [de Morgan] = A + (B'+C)' = [de Morgan] = A + BC$$

GIVEN FORM	DESIRED FORM			
	Minterm Expansion of $f$	Maxterm Expansion of $f$	Minterm Expansion of $f'$	Maxterm Expansion of $f'$
$f = \sum m(3, 4, 5, 6, 7)$	_____	$\prod M(0, 1, 2)$	$\sum m(0, 1, 2)$	$\prod M(3, 4, 5, 6, 7)$
$f = \prod M(0, 1, 2)$	$\sum m(3, 4, 5, 6, 7)$	_____	$\sum m(0, 1, 2)$	$\prod M(3, 4, 5, 6, 7)$

Minterm / maxterm

notation with

-  $\sum m$  (for minterms, sum of products)

-  $\prod M$  (for maxterms, product of sums)

The minterm expansion (sum of products) and maxterm expansion (product of sums) may be found by writing a truth table or by algebraic expansion, as in the following example.



$$= a'(b'+d) + acd'$$

$$\begin{aligned} f &= a'b' + a'd + acd' \\ &= a'b'(c+c')(d+d') + a'd(b+b')(c+c') + acd'(b+b') \\ &= a'b'c'd' + a'b'c'd + a'b'cd' + a'b'cd + a'b'e'd + a'b'ed \\ &\quad + a'bc'd + a'bcd + abcd' + ab'cd' \end{aligned} \quad (4-9)$$

$$\begin{aligned} f &= a'b'c'd' + a'b'c'd + a'b'cd' + a'b'cd + a'bc'd + a'bcd + abcd' + ab'cd' \\ &\quad 0000 \quad 0001 \quad 0010 \quad 0011 \quad 0101 \quad 0111 \quad 1110 \quad 1010 \\ f &= \sum m(0, 1, 2, 3, 5, 7, 10, 14) \end{aligned} \quad (4-10)$$

### Minterm Expansion (p. 89)

$$\begin{aligned} f &= a'(b'+d) + acd' \\ &= (a' + cd')(a + b' + d) = (a' + c)(a' + d')(a + b' + d) \\ &= (a' + bb' + c + dd')(a' + bb' + cc' + d')(a + b' + cc' + d) \\ &= (a' + bb' + c + d)(a' + bb' + c + d')(a' + bb' + c + d)(a' + bb' + c + d) \\ &\quad (a + b' + cc' + d) \\ &= (a' + b + c + d)(a' + b' + c + d)(a' + b + c + d')(a' + b' + c + d') \\ &\quad \begin{matrix} 1000 & 1100 & 1001 & 1101 \\ (a' + b + c + d)(a' + b' + c + d)(a + b' + c + d)(a + b' + c' + d) \\ 1011 & 1111 & 0100 & 0110 \end{matrix} \\ &= \prod M(4, 6, 8, 9, 11, 12, 13, 15) \end{aligned} \quad (4-11)$$

### Maxterm Expansion (p. 90)

Expansion by introduction of missing variables, using  $X + X' = 1 \Rightarrow Y(X + X') = Y$

Expansion by introduction of missing variables, using  $XX' = 0 \Rightarrow Y + XX' = Y$

**Table 4-2. General Truth Table for Three Variables**

A	B	C	F
0	0	0	$a_0$
0	0	1	$a_1$
0	1	0	$a_2$
0	1	1	$a_3$
1	0	0	$a_4$
1	0	1	$a_5$
1	1	0	$a_6$
1	1	1	$a_7$

$$F = a_0m_0 + a_1m_1 + a_2m_2 + \dots + a_7m_7 = \sum_{i=0}^7 a_i m_i$$

**Table 4-3. Conversion of Forms**

	DESIRED FORM			
	Minterm Expansion of $F$	Maxterm Expansion of $F$	Minterm Expansion of $F'$	Maxterm Expansion of $F'$
GIVEN FORM	Minterm Expansion of $F$	maxterm nos. are those nos. not on the minterm list for $F$	list minterms not present in $F$	maxterm nos. are the same as minterm nos. of $F$
	Maxterm Expansion of $F$	minterm nos. are those nos. not on the maxterm list for $F$	minterm nos. are the same as maxterm nos. of $F$	list maxterms not present in $F$

# Incompletely specified functions (Section 4.5)

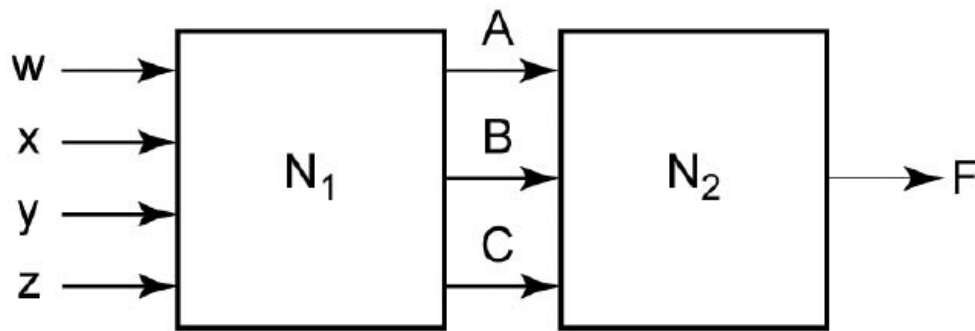


Table 4-5. Truth Table with Don't Cares


A	B	C	F	(1)	(2)	(3)
0	0	0	1			
0	0	1	X	0	1	1
0	1	0	0			
0	1	1	1			
1	0	0	0			
1	0	1	0			
1	1	0	X	0	0	1
1	1	1	1			

Section 4.5, p. 93

*N1 does not generate these configurations*

- (1) all  $x=0$ :  $F = A'B'C' + A'BC + ABC = A'B'C' + BC$
- (2)  $F = A'B'C' + A'B'C + A'BC + ABC = A'B' + BC$
- (3)  $F = A'B'C' + A'B'C + A'BC + ABC' + ABC = A'B' + A'BC + AB = A'[B' + BC] + AB = A'[B' + C] + AB = A'B' + A'C + AB$

# Design of an adder (Example 2 section 4.6)

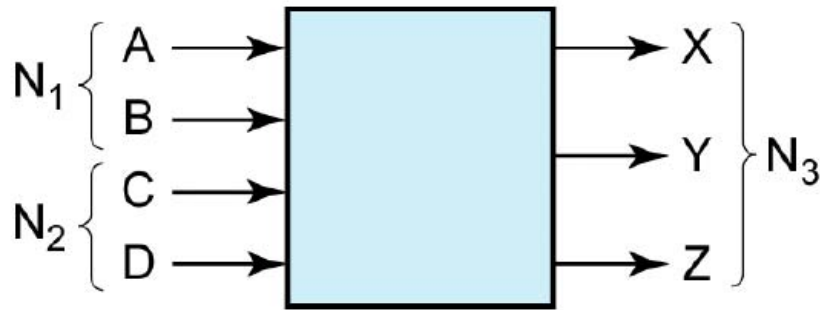

Section 4.6, p. 95

TRUTH TABLE:

N <sub>1</sub>		N <sub>2</sub>		N <sub>3</sub>		
A	B	C	D	X	Y	Z
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	1	0	0
1	0	0	1	1	0	1
1	0	1	0	1	1	0
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	0
1	1	1	0	1	1	0
1	1	1	1	1	1	1

TRUTH TABLE:

N <sub>1</sub>		N <sub>2</sub>		N <sub>3</sub>		
A	B	C	D	X	Y	Z
1	0	0	0	0	1	0
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Section 4.6, p. 95

E.g.,

$$\begin{array}{r}
 N_1 = \text{[yellow box]} \quad A \ B \\
 + N_2 = \text{[yellow box]} \quad C \ D \\
 \hline
 N_3 = \text{[yellow box]} \quad X \ Y \ Z
 \end{array}$$

$$X(A, B, C, D) = \sum m(7, 10, 11, 13, 14, 15)$$

$$Y(A, B, C, D) = \sum m(2, 3, 5, 6, 8, 9, 12, 15)$$

$$Z(A, B, C, D) = \sum m(1, 3, 4, 6, 9, 11, 12, 14)$$

## Design of Binary Adders (4.7)

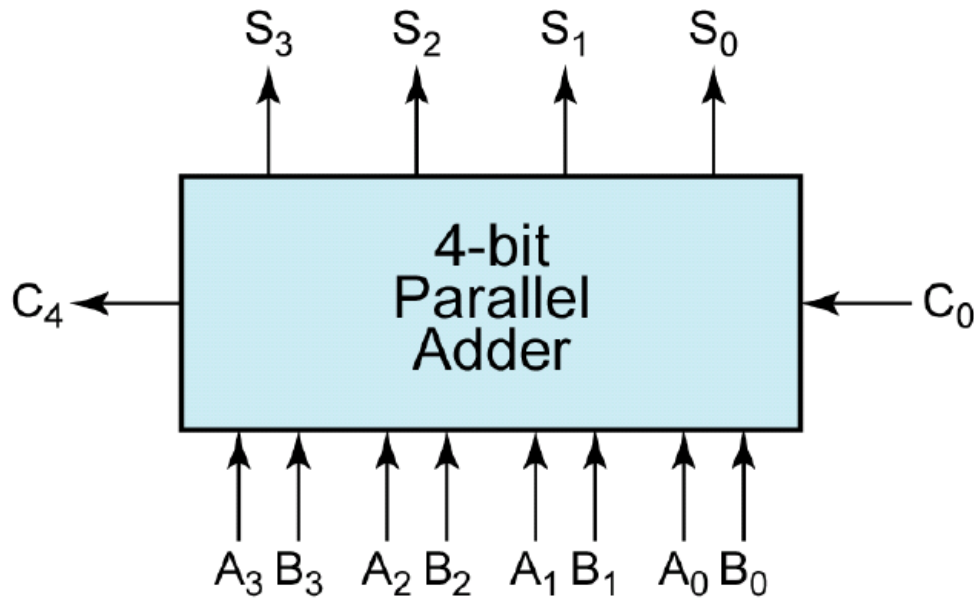


Figure 4-2: Parallel Adder for 4-Bit Binary Numbers

This circuit has  
nine inputs — too big!


Add two 4-bit unsigned  
numbers, giving a  
4-bit number as result.

Also, allow a 1-bit carry  
as input and a one-bit  
carry as output

$$\begin{array}{r} \phantom{+} \phantom{A_3} \phantom{A_2} \phantom{A_1} C_0 \\ + \phantom{A_3} A_2 \phantom{A_2} A_1 \phantom{A_0} \\ + \phantom{A_3} B_3 \phantom{B_2} B_1 \phantom{B_0} \\ \hline C_4 \phantom{S_3} S_2 \phantom{S_1} S_0 \end{array}$$

Instead, connect four full adders.

Ex.:

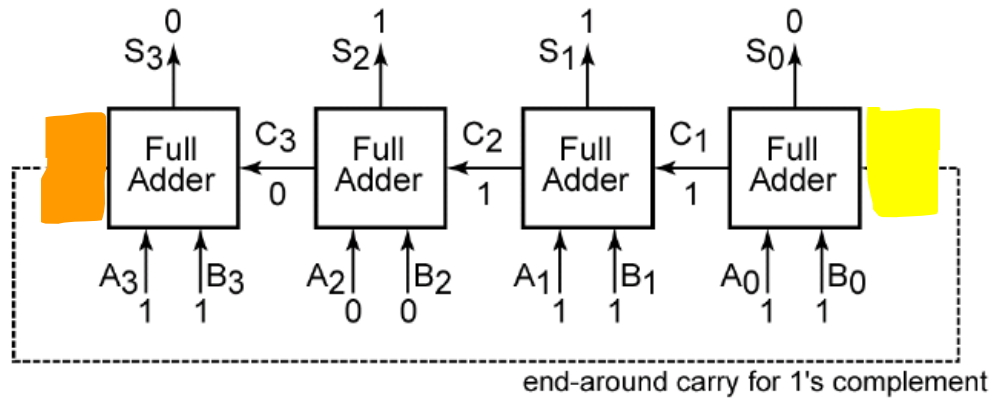

$$\begin{array}{r}
 \phantom{+} 1011 \\
 + 1011 \\
 \hline
 10110
 \end{array}
 \begin{array}{l}
 = A_3 A_2 A_1 A_0 \\
 = B_3 B_2 B_1 B_0 \\
 = S_3 S_2 S_1 S_0
 \end{array}$$

**Figure 4-3: Parallel Adder Composed of Four Full Adders**

Each full adder adds two one-bit numbers and a carry, and produces one one-bit number and a carry.

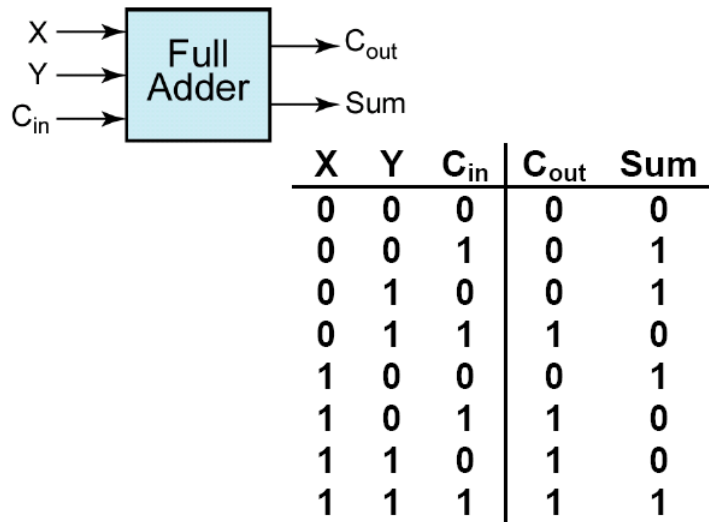



Figure 4-4: Truth Table for a Full Adder

$$\begin{aligned}
 \text{Sum} &= \sum m(1, 2, 4, 8) = \\
 &= X'Y'C_{in} + X'Y C_{in} + XY' C_{in} + XY C_{in} = \\
 &= X' (Y'C_{in} + Y C_{in}) + X (Y' C_{in} + Y C_{in}) = \\
 &= X' (Y \oplus C_{in}) + X (Y \equiv C_{in}) = \\
 &= X' (Y \oplus C_{in}) + X (Y \oplus C_{in})' = \\
 &= X \oplus (Y \oplus C_{in}) = \{3-13\} : \text{associativity}
 \end{aligned}$$

of exclusive-or) =  $X \oplus Y \oplus C_{in}$

$$\begin{aligned}
 C_{out} &= \sum m(3, 5, 6, 7) = X'Y C_{in} + XY' C_{in} + XY C_{in}' + XY C_{in} = \\
 &= (X'Y C_{in} + XY' C_{in}) + (XY C_{in}' + XY C_{in}) = \\
 &= Y C_{in} + X C_{in} + XY
 \end{aligned}$$

Here are the resulting circuits:

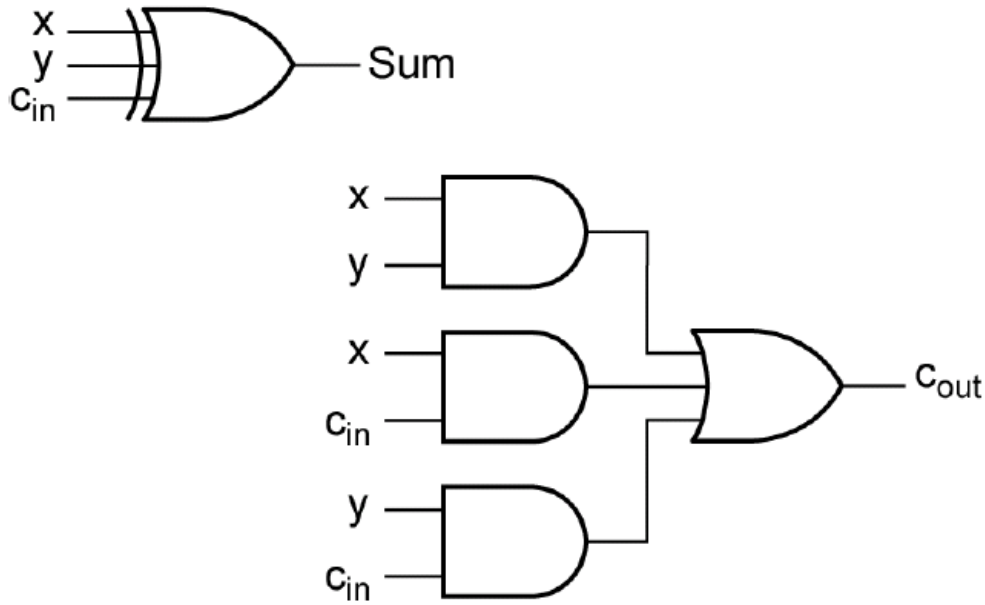

**Figure 4-5: Implementation of Full Adder**