
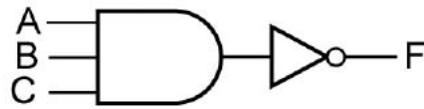


 

(a) 3-input NAND gate




(b) NAND gate equivalent



(c) n-input NAND gate

Figure 7-8: NAND Gates


Ch. 7 text
AND-NOT

 

$$F = (\text{from (a)}) = (A \cdot B \cdot C)' =$$

$$= (\text{De Morgan's Law}) =$$


$$A' + B' + C' = (\text{from (d)}) = F$$

 


(d) is a shorthand for (e).



(a) 3-input NOR gate

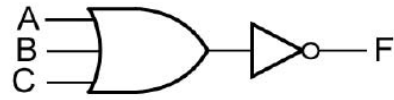

(b) NOR gate equivalent

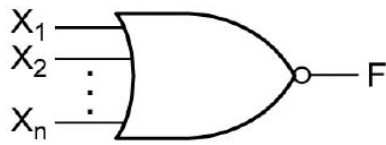

(c) n-input NOR gate

 
 


Figure 7-9: NOR Gates


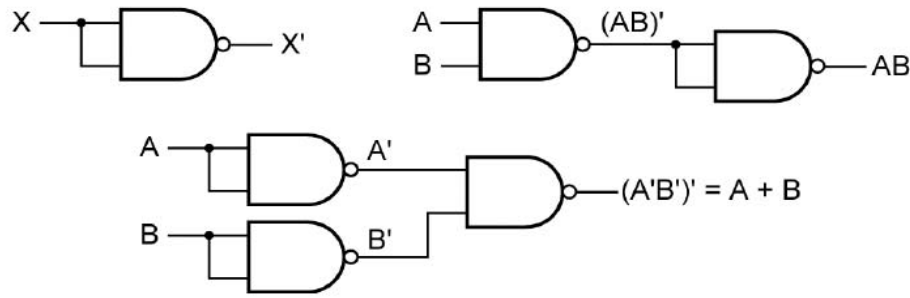


Figure 7-10: NAND Gate Realization of NOT, AND, and OR


$\{ \text{NAND} \}$ is a complete set of Boolean gates, i.e. this set is sufficient to realize any Boolean circuit.

We know that $\{ \text{AND}, \text{OR}, \text{NOT} \}$ is sufficient.

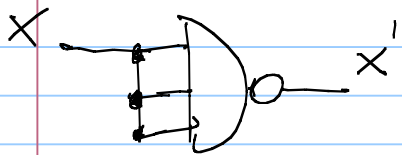NAND, as shown in the figure above, can realize NOT, AND, and OR. So, $\{ \text{NAND} \}$ is also a complete set of Boolean gates.



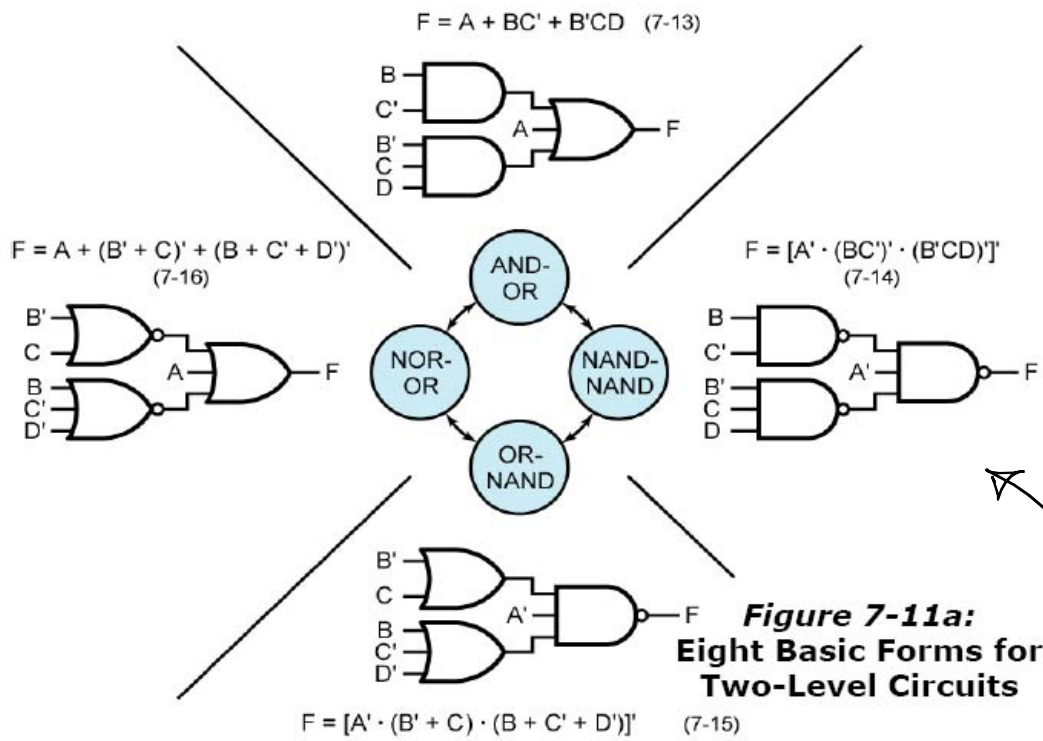An inverter built from a 3-input NAND.
 $(X \cdot X \cdot X)' = X'$



©2004 Brooks/Cole

SOP realization on top
Start from SOP

$$F = A + BC' + B'CD =$$

$$[(A + BC' + B'CD)']' =$$

$$[A' \cdot \boxed{(BC)'} \cdot (B'CD)']' =$$

NAND(B, C')

Start with POS
(instead of SOP)



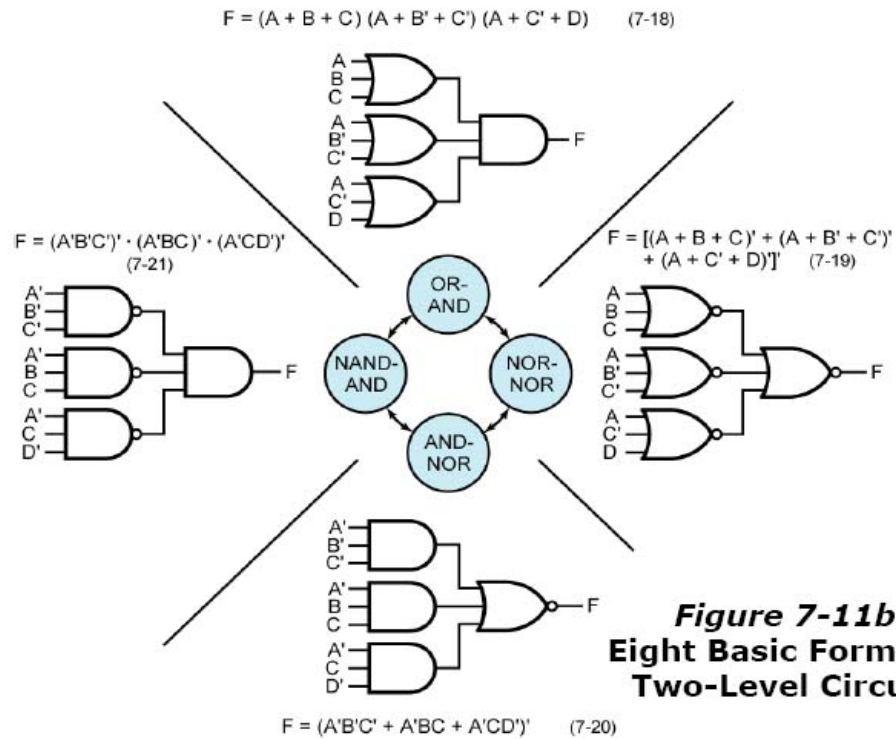


Figure 7-11b:
Eight Basic Forms for
Two-Level Circuits

Circuit 2 Discussion

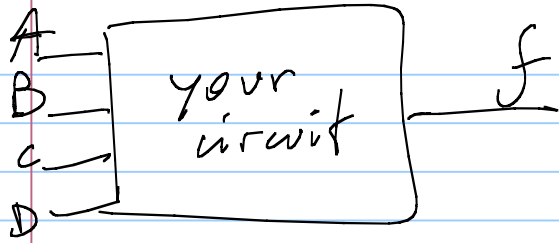

$$f' = g(A, B, C, D)$$

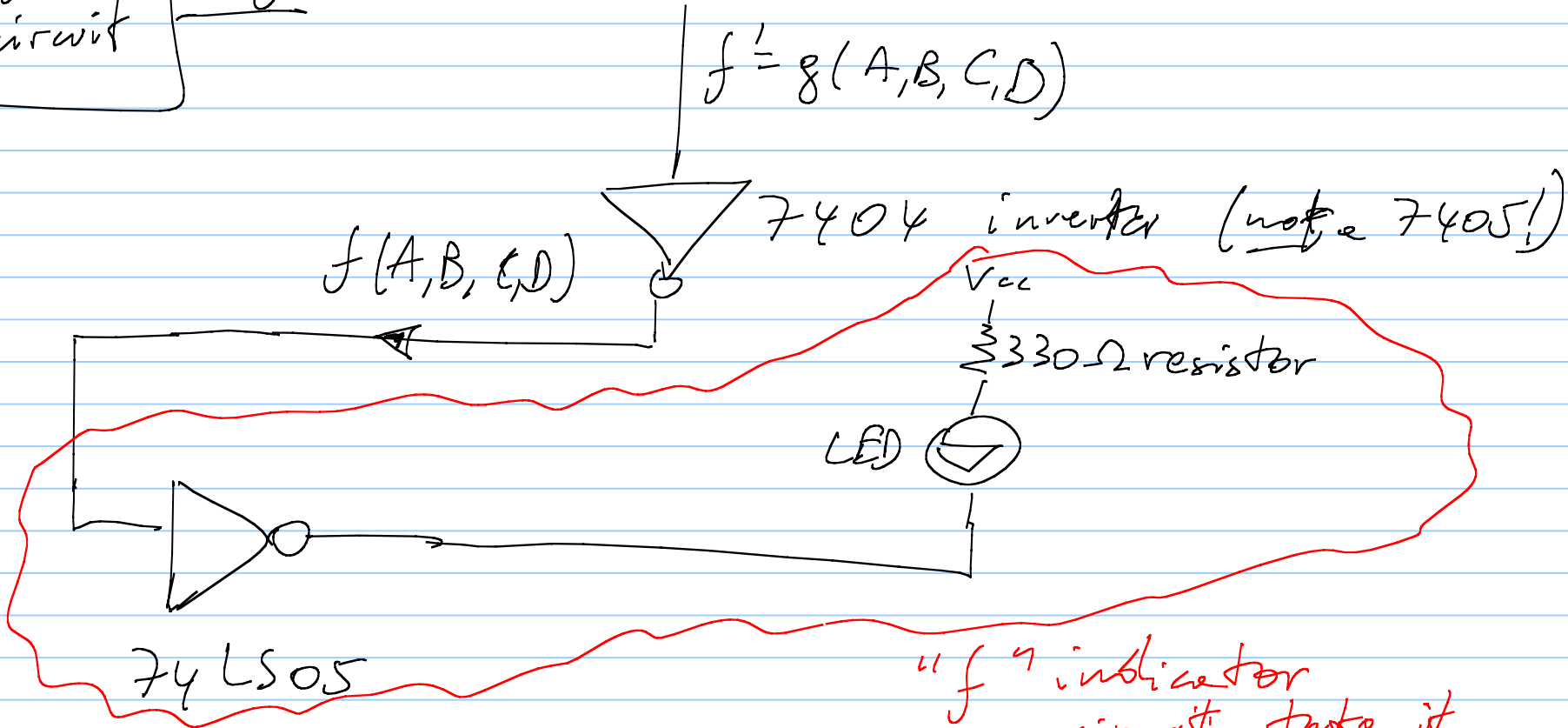

74LS05

"f" indicator circuit - take it as a black box!

- (1) Design a ^{minimal} SOP (AND-OR) expression for g using a K-map
 - (2) Design the corresponding NAND-NAND circuit
 - (3) Negate the output with a 7404 inverter
 - (4) The output of the 7404 inverter will be displayed using the LED indicator circuit.
- (3) and (4) are on the previous page

$$f(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 6) + \sum d(10, 11, 12, 13, 14, 15)$$

		A			
		00	01	11	10
00	0	1	1	X	0
	1	1	1	X	0
01	3	1	0	X	X
	2	1	1	X	X

B


D

	00	01	11	10
	0	4	12	8
00	0	0	X	1
01	1	5	X	9
11	3	7	X	11
10	2	6	X	10

B




$$g(A, B, C, D) = f'(A, B, C, D) =$$
 
$$\sum m(7, 8, 9) + \sum \phi(10, 11, 12, 13, 14, 15)$$




The K-map for g



$$g = A + BCD$$

   

From SOP (AND-OR) to NAND-NAND

 


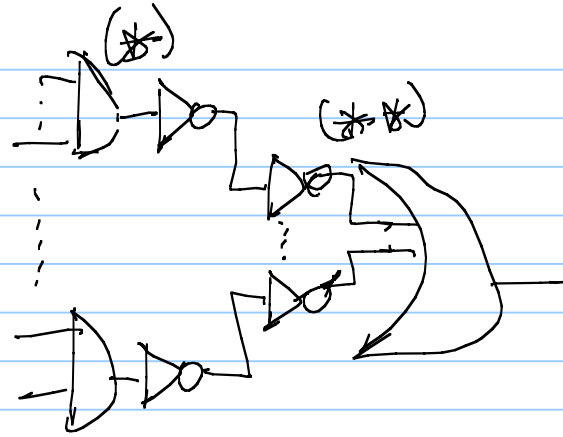 negate
both the
outputs
of the AND
gates and
the inputs of
the OR gate





$$(*) = (**)$$

rotationally equivalent to;

 

De Morgan's
law

 

 

$$f(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 6) + \sum d(10, 11, 12, 13, 14, 15)$$

$$f = A'D' + A'B' + A'C'$$

Check that $g' = f$

$$g' = (A + BCD)' = A' \cdot (BCD)' =$$

$$= A' \cdot (B' + C' + D') = A'B' + A'C' + A'D' = f \quad \checkmark$$


prime implicants:

	m_0	m_1	m_2	m_3	m_4	m_5	m_6
$A'C'$	X	X					
$A'B'$	X	X	X				
$A'D'$	X		X				
BD'							
CB'			X				

(Quine-McCluskey algorithm from ch. 6)

none of the 1s is covered by only one implicant! So there are no essential prime implicants

 How many configurations of 4 bin. vars? 16
How many Boolean functions of 4 binary variables?
or 1



$$A: 2^{16}$$