

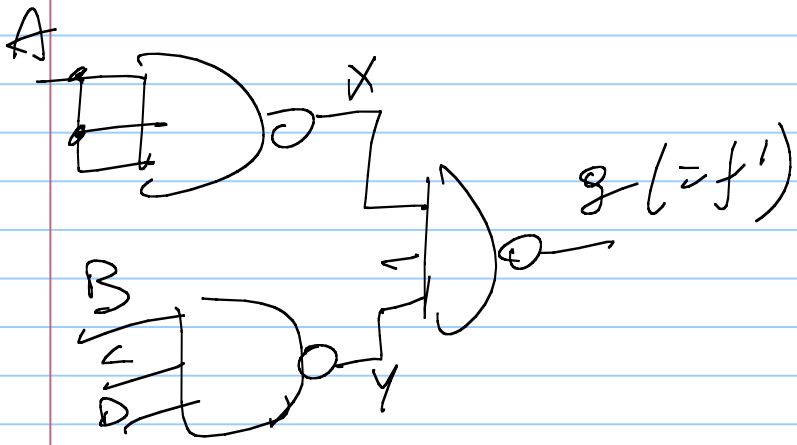


Circuit 2

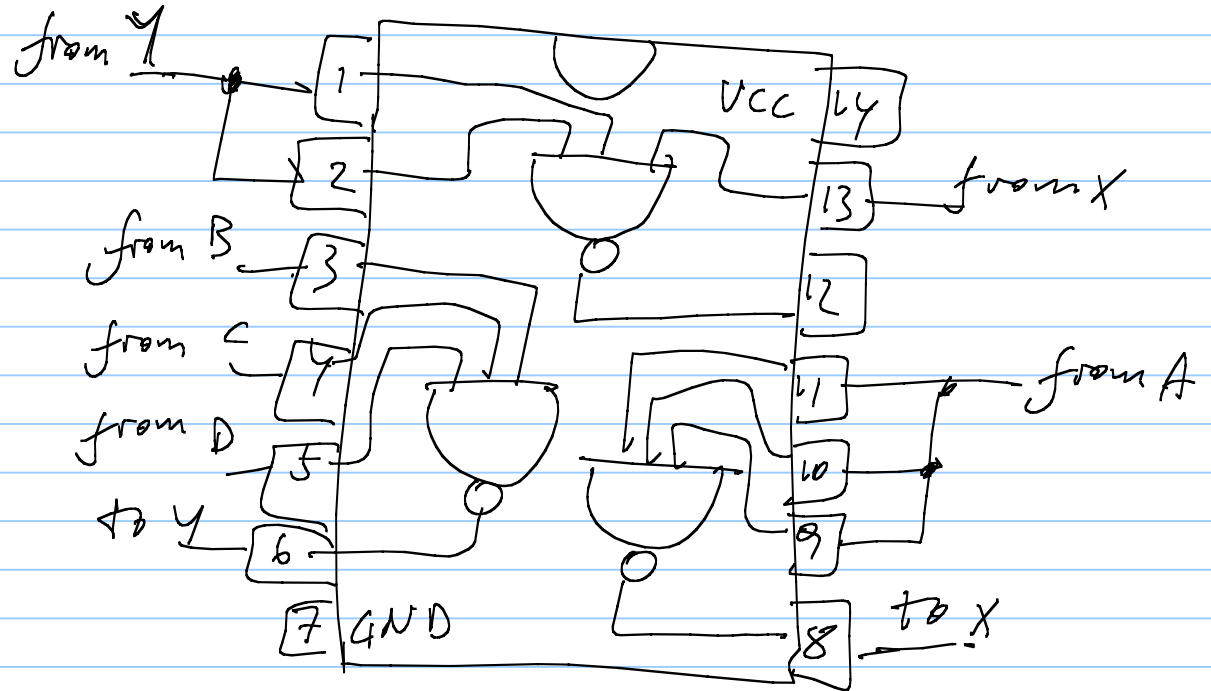


Mr. Warren
Mr. Evans

	A	B	C	D	f	g=f'
m ₀	0	0	0	0	1	0
m ₁	0	0	0	1	1	0
m ₂	0	0	1	0	1	0
m ₃	0	0	1	1	1	0
m ₄	0	1	0	0	1	0
m ₅	0	1	0	1	1	0
m ₆	0	1	1	0	1	0
m ₇	0	1	1	1	0	1
m ₈	1	0	0	0	0	1
m ₉	1	0	0	1	0	1
m ₁₀	1	0	1	0	0	1
m ₁₁	1	0	1	1	0	1
m ₁₂	1	1	0	0	0	1
m ₁₃	1	1	0	1	0	1
m ₁₄	1	1	1	0	0	1
m ₁₅	1	1	1	1	0	1

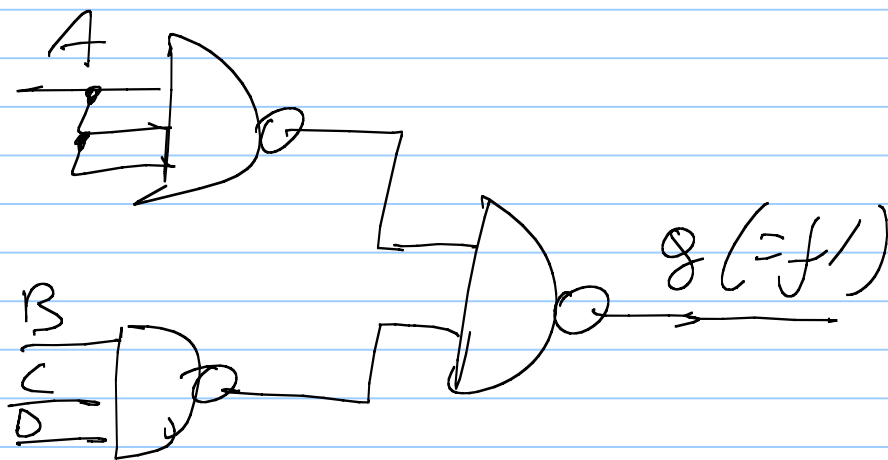

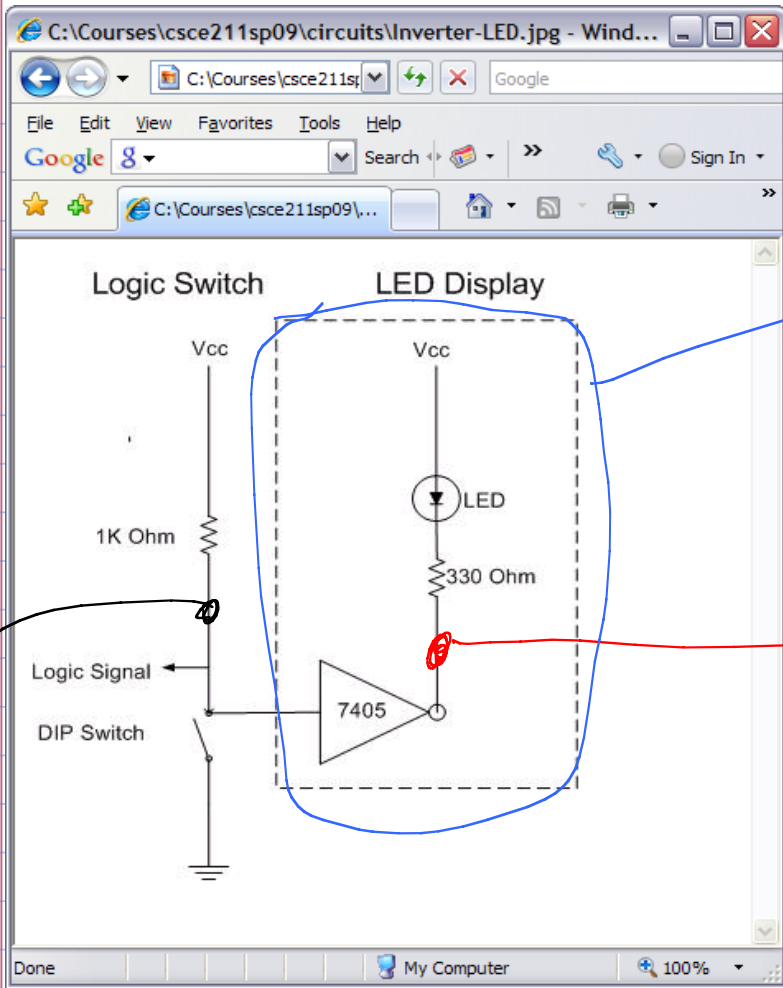Three NAND gates
 from the 7410 chip.
 which has three NAND gates



Either solution is acceptable.
Some pros & cons are described below.

This is a buffer-driven circuit

Sorry - see below!

Take inputs for circuit 2 here

No - do not fool with the output of an open collector.

Do not take them here - several of you did this.
Please redo & bring your circuit on Friday, April 3!

Each input is 1 when the corresponding DIP switch is OFF
 • when the corresponding LED is lit

Q8

$$(A+B)' = (A'+B')' = (A')' \cdot (B')' = AB$$

De Morgan's Law: $(X+Y)' = X'Y'$

Quine-McCluskey Algorithm
 Ch. 7 text

$$f(a, b, c, d) = \sum m(0, 1, 2, 5, 6, 7, 8, 9, 10, 14)$$

group 0	0	0000
group 1	1	0001
	2	0010
	8	1000
group 2	5	0101
	6	0110
	9	1001
	10	1010
group 3	7	0111
	14	1110

Equation (6-2)

Group minterms by how many
 1s they have

Table 6-1. Determination of Prime Implicants

	Column I	Column II	Column III
group 0	0 0000 ✓	0, 1 000- ✓	0, 1, 8, 9 -00-
group 1	1 0001 ✓	0, 2 00-0 ✓	0, 2, 8, 10 -0-0
	2 0010 ✓	0, 8 -000 ✓	0, 8, 1, 9 -00-
	8 1000 ✓	1, 5 0-01	0, 8, 2, 10 -0-0
group 2	5 0101 ✓	1, 9 -001 ✓	2, 6, 10, 14 --10
	6 0110 ✓	2, 6 0-10 ✓	2, 10, 6, 14 --10
	9 1001 ✓	2, 10 -010 ✓	
	10 1010 ✓	8, 9 100- ✓	
group 3	7 0111 ✓	8, 10 10-0 ✓	
	14 1110 ✓	5, 7 01-1	
		6, 7 011-	
		6, 14 -110 ✓	
	10, 14 1-10 ✓		

Table 6-2. Prime Implicant Chart

		0	1	2	5	6	7	8	9	10	14
(0, 1, 8, 9)	$b'c'$	X	X					X	X		
(0, 2, 8, 10)	$b'd'$	X		X				X		X	
(2, 6, 10, 14)	cd'			X		X				X	X
(1, 5)	$a'c'd$		X		X						
(5, 7)	$a'bd$				X		X				
(6, 7)	$a'bc$					X	X				

$$b'c' + cd' + a'bd$$

Table 6-5.

			0	1	2	5	6	7
P_1	(0, 1)	$a'b'$	X	X				
P_2	(0, 2)	$a'c'$	*		*			
P_3	(1, 5)	$b'c$		X		X		
P_4	(2, 6)	bc'			X		X	
P_5	(5, 7)	ac				X		X
P_6	(6, 7)	ab					X	X

no essential prime implicant
 Every column has at least two crosses; every minterm can be covered by at least two prime implicants.

Patrick's method Note: a similar technique has applications outside of digital logic design.

Label the prime implicants by P_i , $1 \leq i \leq n$ (n is the number of prime implicants, as in the example of Table 6-5). Since all minterms must be covered,

the following expression is true:

$$F = (P_1 + P_2)(P_1 + P_3)(P_2 + P_4)(P_3 + P_5)(P_4 + P_6)(P_5 + P_6)$$

$$\text{Use } x + yz = (x + y)(x + z)$$

(p. 61 book)

$$P = (P_1 + P_2 P_3)(P_4 + P_2 P_6)(P_5 + P_3 P_6) =$$

$$= (P_1 P_4 + P_1 P_2 P_6 + \dots)$$

$$= P_1 P_4 P_5 + P_1 P_2 P_5 P_6 + P_2 P_3 P_4 P_5 + P_1 P_3 P_4 P_6 + P_2 P_3 P_6$$

↙

$$a'b' + bc' + ac$$

↘

$$a'c' + b'c + ab$$