
 


Take-home Test 2 due Friday, April 17

Latches and flip-flops (Ch 11)

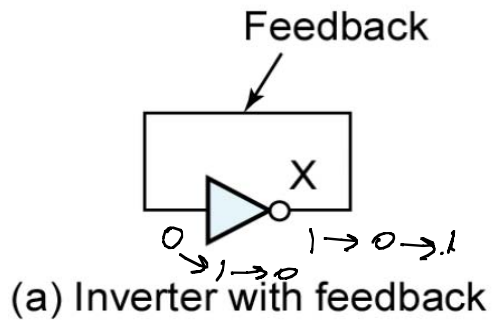Sequential circuits are circuits with memory, i.e., the output of a sequential circuit depends not only on the current input, but also on the sequence of previous inputs.



(b) Oscillation at inverter output

Figure 11-1

To get memory, we use feedback.

In this circuit, feedback is used, but there is no memory!

 
 


Figure 11-2

This circuit (with feedback) has two stable states.
(a) and (b)

 
 
 
 


Figure 11-4

In a latch, there is no separate clock input; in a flip-flop, there is.

(a) is a stable configuration. In (b), we take (a) and change S to 1. The circuit moves to the new configuration displayed in (b). This configuration

(is stable.) Change S back to 0. Surprise! P and Q remain the same, and 11-4(a) is stable!

Change R to 1, Q changes to 0 and P changes to 1, and 11-4(b) is stable.

$R=S=1$ is not allowed.

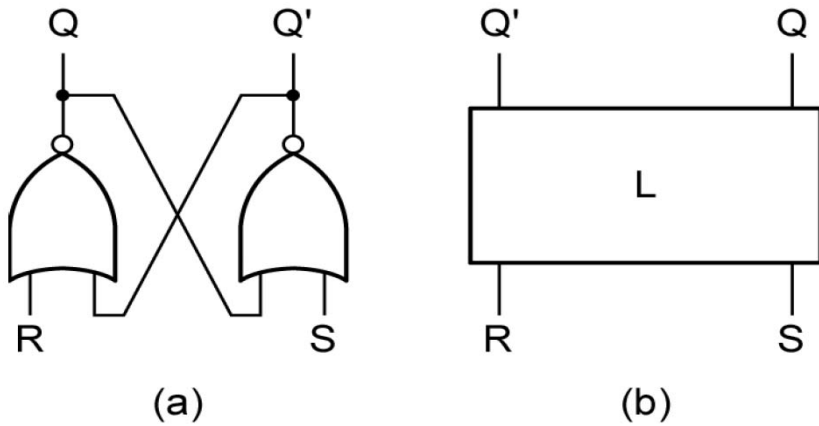


Figure 11-5: S-R Latch

(a) is the cross-coupled form of the S-R latch circuit
(b) is the gate symbol for the S-R latch

When $S=R=1$, the latch oscillates. $S=R=1$ is therefore not allowed as an input.

 


Figure 11-6: Improper S-R Latch Operation

 


Figure 11-7: Timing Diagram for S-R Latch

current state \downarrow next state \downarrow

$S(t)$	$R(t)$	$Q(t)$	$Q(t + \epsilon)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	—
1	1	1	—

} inputs not allowed
from 11-3(e) to 11-3(b)

Table 11-1. S-R Latch Operation

R(t) Q(t) \ S(t)		S(t)	
		0	1
R(t) Q(t)	00	0	1
	01	1	1
	11	0	X
	10	0	X

$$Q(t + \epsilon) = S(t) + R'(t) Q(t)$$

Figure 11-8: Map for $Q(t + \epsilon)$

$$Q^+ = S + R'Q \quad (SR=0)$$

↑ next state ↑ current state ↑ $S=R=0$ is not allowed

characteristic equation
or next-state equations
of the S-R latch

We will see several other latches & flip-flops and their characteristic equations!