

 


# Some hints for test 2 (take-home test)

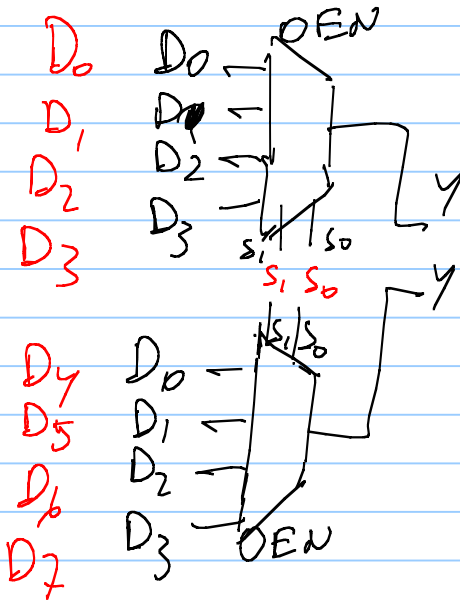

$S_2$



 


Circuit 3 will be posted before next class  
 It will be due Wednesday of next week.

**This chapter in the book includes:**

- Objectives
- Study Guide
- 11.1 Introduction
- 11.2 Set-Reset Latch
- 11.3 Gated D Latch
- 11.4 Edge-Triggered D Flip-Flop
- 11.5 S-R Flip-Flop
- 11.6 J-K Flip-Flop
- 11.7 T Flip-Flop
- 11.8 Flip-Flops with Additional Inputs
- 11.9 Summary
- Problems
- Programmed Exercise

We already analyzed the Set Reset Latch

   

Delays in timing diagram

**Tabella delle transizioni**

SR	00	01	11	10
Q	0	0	-	1
1	1	0	-	1


→

S	R	Q*
0	0	Q
0	1	0
1	0	1
1	1	-

Tabella delle eccitazioni

Q	Q*	S	R
0	0	0	-
0	1	1	0
1	0	0	1
1	1	-	0

Diagramma Temporale

 

**Espressione logica**


$Q^* = S + R'Q$   
 Con vincolo  $S=R \neq 1$

Q\*: stato prossimo  
 Q: stato presente

Four different description of the behavior of the S-R latch


not in Ch. 11 of our textbook

[Sammi]

 


**Figure 11-9: Switch Debouncing with an S-R Latch**

  After this short delay, the output of this debounced double throw switch stays at 1, even though S bounces between 1 and 0.



(a)



(b)

$\bar{S}$	$\bar{R}$	$Q$	$Q^+$
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	-
0	0	1	-

} inputs not allowed

Figure 11-10:  $\bar{S}$ - $\bar{R}$  Latch

Deal of  
S-R latch

# Gated D Latch

 


Figure 11-11: Gated D Latch

GDQ	Q <sup>+</sup>
000	0
001	1
010	0
011	1
100	0
101	0
110	1
111	1



Figure 11-12 (left): Symbol and Truth Table for Gated Latch

GD	00	01	11	10
0	0	0	1	0
1	1	1	1	0

$Q^+ = G'Q + GD$

Figure 11-12 (continued)

  Characteristic equation of the gated D latch. When  $G=1$ , the input D is passed "transparently" to the Q output. When  $G=0$ , there is no state change.



(b) Falling-edge trigger

D	Q	Q <sup>+</sup>
0	0	0
0	1	0
1	0	1
1	1	1

(c) truth table

 
$$Q^+ = D$$

Figure 11-13: D Flip-Flops

In a flip-flop, the output only changes in response to the clock transitioning from 0 to 1 ("rising-edge trigger") or 1 to 0 ("falling edge trigger").


0 → 1 transition

 1 → 0 transition

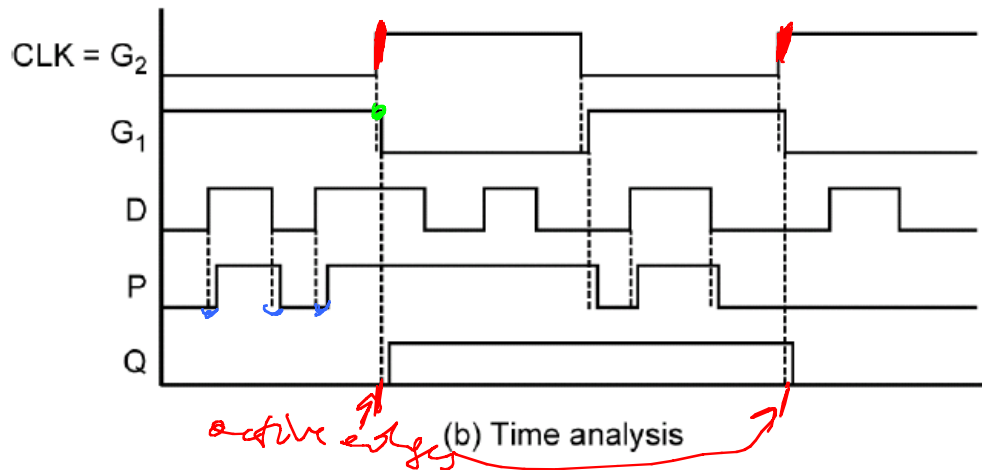


**Figure 11-14: Timing for D Flip-Flop (Falling Edge Trigger)**

Timing is critical for flip-flops!




(a) Construction from two gated D latches



**Figure 11-15: D Flip-Flop (Rising Edge Trigger)**



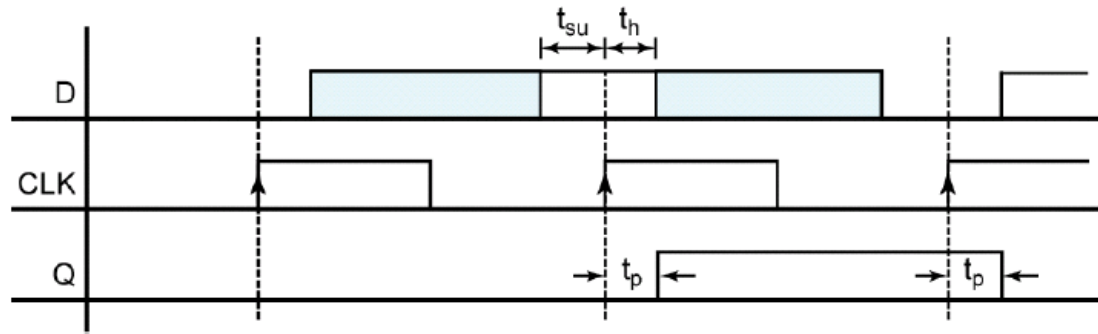


**Figure 11-16: Setup and Hold Times for an Edge-Triggered D Flip-Flop**

$t_p$  is the propagation delay time, from the time the clock changes to the time the output Q changes.


$t_{su}$ : setup time - time that D must be stable before the active edge of the clock

$t_h$ : hold time - time that D must be stable after the active edge of the clock

 
If setup and hold times are not respected, the flip-flop behavior is unpredictable.




(a) Simple flip-flop circuit

 

(b) Setup time not satisfied

 

(c) Setup time satisfied

 

(d) Minimum clock period

**Figure 11-17: Determination of Minimum Clock Period**


5 ns propagation delay for f-f  
3 ns setup time for f-f

2 ns propagation delay for the inverter

$$(b) 9 \text{ ns } (4 + 5)$$

$$(c) 15 \text{ ns } (7 + 8)$$

$$(d): 10 \text{ ns } (5 + 5)$$

 


Operation summary:


- S = R = 0    no state change
- S = 1, R = 0    set Q to 1 (after active Ck edge)
- S = 0, R = 1    reset Q to 0 (after active Ck edge)
- S = R = 1    not allowed

Figure 11-18: S-R Flip-Flop

$$Q^+ = S + R'Q \quad (SR=0)$$

 


(a) Implementation with two latches

 

(b) Timing analysis

Figure 11-19: S-R Flip-Flop Implementation and Timing

active clock edges

 

(a) J-K flip-flop


$$Q^+ = JQ' + K'Q$$

JKQ	Q <sup>+</sup>
000	0
001	1
010	0
011	0
100	1
101	1
110	1
111	0

*S-R flop behavior*

Figure 11-20ab: J-K Flip-Flop (Q Changes on the Rising Edge)

©2004 Brooks/Cole

 

(c) J-K flip-flop timing

Figure 11-20c: J-K Flip-Flop (Q Changes on the Rising Edge)

 


Figure 11-21: Master-Slave J-K Flip-Flop (Q Changes on Rising Edge)

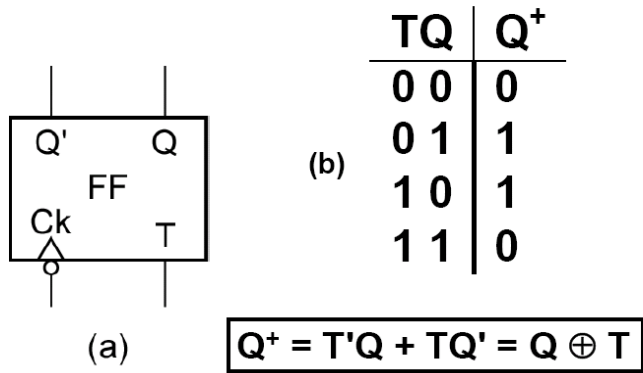


Figure 11-22ab: T Flip-Flop


 



Figure 11-23: Timing Diagram for T Flip-Flop (Falling-Edge Trigger)

 

(a) Conversion of J-K to T    (b) Conversion of D to T

Figure 11-24: Implementation of T Flip-Flops

T for Toggle

 

CK	D	PreN	ClrN	Q <sup>+</sup>
x	x	0	0	(not allowed)
x	x	0	1	1
x	x	1	0	0
↑	0	1	1	0
↑	1	1	1	1
0,1, ↓	x	1	1	Q (no change)

Figure 11-25: D Flip-Flop with Clear and Preset



 



Figure 11-26: Timing Diagram for D Flip-Flop with Asynchronous Clear and Preset

 

(a) Gating the clock

 

(b) D-CE symbol

 

(c) Implementation

Figure 11-27: D Flip-Flop with Clock Enable