

Note on Problem 1 of Take-home Test 2

1		X	X
	1	X	
1			1
1	1		X

$B'D'$ is an essential prime
implicant.

Registers (ch. 12) are simple sequential circuits.


They are simple enough that the general techniques of Chs 13-16 are not used to analyze and design them.

Registers - memorize a fixed amount of information

- they operate on their contents as follows
 - shift (right or left)
 - load (parallel or serial)
 - retrieve (read)

Register example images are from M.G. Sami's course web site (mentioned before).

 
- Registro *parallelo-parallelo*
 - Esempio di registro a 4 bit.



A 4-bit
Parallel-parallel register


No shifting allowed

 - Registro *serie-serie* (Shift Register - Registro a Scorrimento)
 - Esempio di registro a 4 bit



Shifts one bit to
the right at every
active clock signal.
Leftmost bit is replaced by
the register input; rightmost
bit is lost

 - Registro *serie-parallelo*
 - Esempio di registro a 4 bit




4-bit serial-parallel register

input is serial; output is parallel.

This is a shift register, with

shifting done as in the previous register.

 - Registro *parallelo-serie*
 - Esempio a 4 bit con scorrimento aritmetico (Shift Destro): In fase di traslazione, ricopia il bit più significativo nella posizione più significativa (estensione del segno)




4-bit right-shift parallel-serial register with persistent sign (MSB)

Note use of 2-to-1 MUX.

Note feedback line

□ Registro circolare a 4 bit

 
- Esempio a 4 bit con rotazione a destra: In fase di traslazione, trasferisce il bit meno significativo al posto di quello più significativo, spostando i rimanenti di una posizione a destra.



4-bit circular register

Note feedback line.

Ch. 13: Analysis of Clocked Sequential Circuits

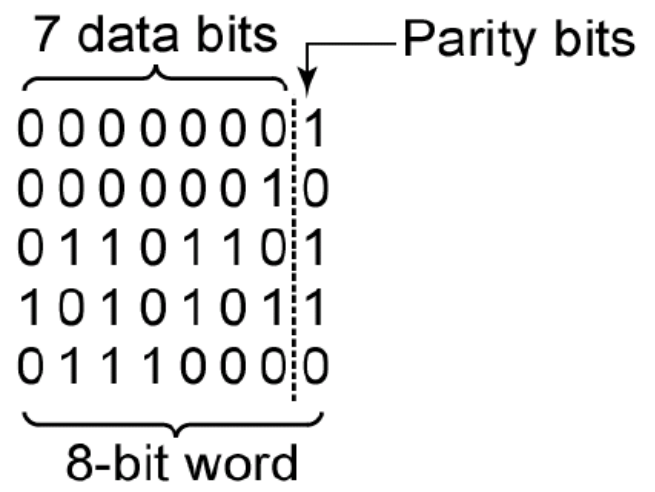

Section 13.1, p. 362

Including the parity bit

Parity is odd when a correct string has an odd number of 1s
Parity is even when a correct string has an even number of 1s.

The resulting code can detect errors in one bit.

The example here is for an odd-parity code.

We are going to design a sequential parity checker

 


Figure 13-1: Block Diagram for Parity Checker

 


Figure 13-2: Waveforms for Parity Checker

 


Figure 13-3: State Graph for Parity Checker

The output Z is a function of the state S (S_0 or S_1) only: this sequential circuit is a Moore machine.

Table 13-1: State Table for Parity Checker

(a)

Present State	Next State		Present Output
	$X = 0$	$X = 1$	
S_0	S_0	S_1	0
S_1	S_1	S_0	1

(b)

Q	Q^+		T		Z
	$X = 0$	$X = 1$	$X = 0$	$X = 1$	
0	0	1	0	1	0
1	1	0	0	1	1

 


Figure 13-4: Parity Checker