



CSCE 611

High-level Digital Systems Design

2004/2/4

Lecture 11 (Design Lab)


ASM Design/Analysis using Logic Synthesis

© 2002 Dr. James P. Davis

Lecture 11 - Outline

- Introduction.
 - ✓ The Ripple and Ring Counters – analysis and design, and logic synthesis to evaluate architectures.
 - ✓ This is a lead-in to the Lab session for Friday's class.
- Analysis & Design methods.
 - ✓ Gate-level sequential machine analysis.
 - ✓ Gate-level to Register-level abstraction.
 - ✓ Register-level design.
 - ✓ Logic Synthesis and comparison of different design architectures.
- Lab
 - ✓ Take each of the three design architectures discussed in class, create models and evaluate the circuit architectures using logic synthesis.


Lab Exercise – Modulo Counter Design

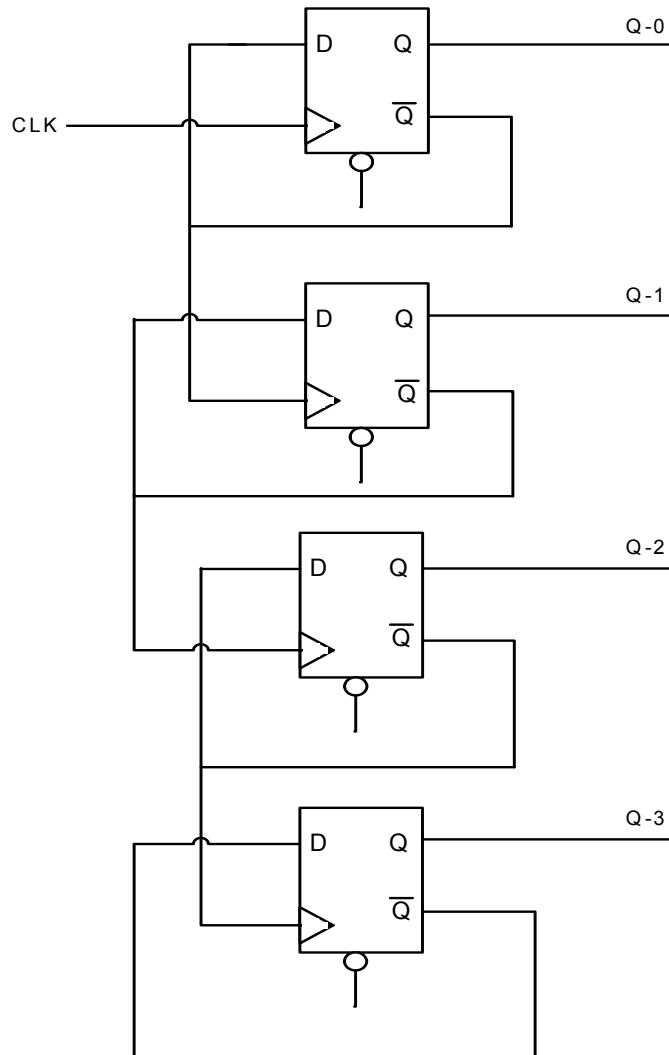

- Gate-level counter:

- ✓ Modulo counters can be implemented using D-Flip Flop “ripple chains”.
- ✓ A single-bit register FF encodes and outputs one of n binary digits, from 0 to digit $n-1$.
- ✓ Arrangement of the bit registers has inverted output \overline{Q}_k of lower counter FF k feeding input of register FF k and clock input of FF $k+1$, up to $n-1^{th}$ FF location $\{k = 0 \text{ to } n-1\}$.
- ✓ The inverted $n-1^{th}$ FF is fed back to its D input (inverting its input each time it is clocked).

Mod-10 Ripple Counter – Architecture #1

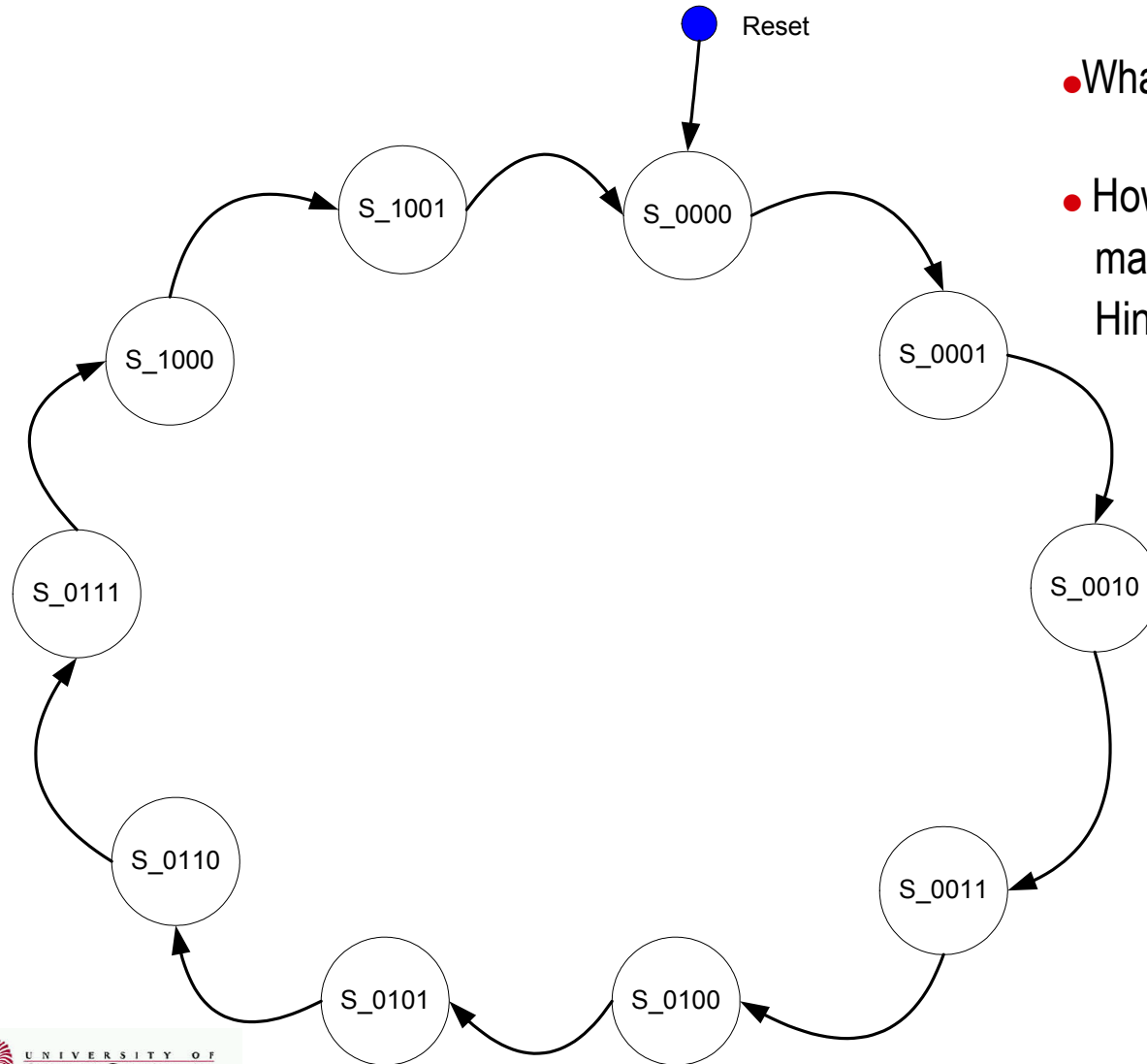


- What about the unused states?
- How would we change this to make it more generic (i.e., Mod-n)? Hint, see Architecture #2.

Laboratory ASM Worksheet



Thread_1

 - Use this worksheet to hand-draw your initial ASM design.



Progr. Mod-n Ripple Counter – Architecture #2


- Mod-n 4-bit Ripple Counter

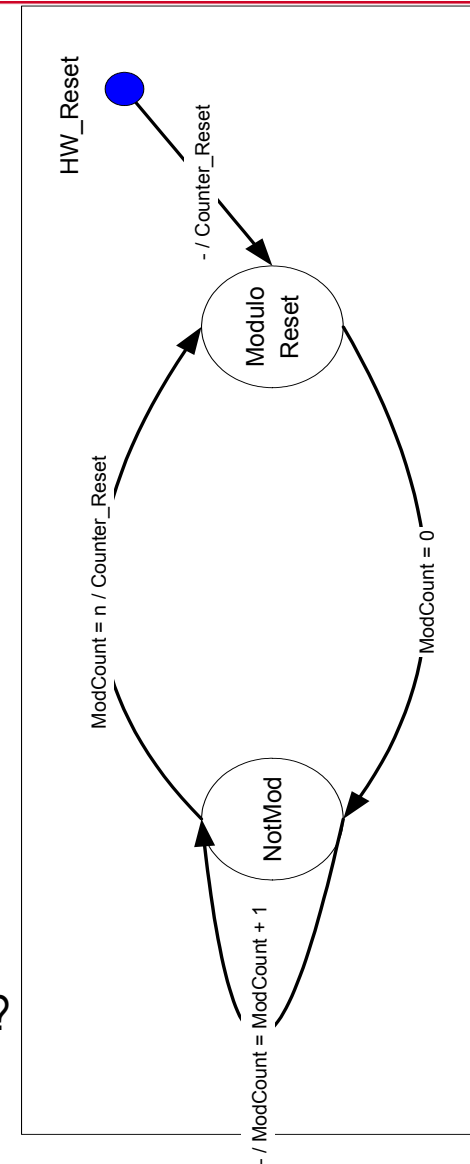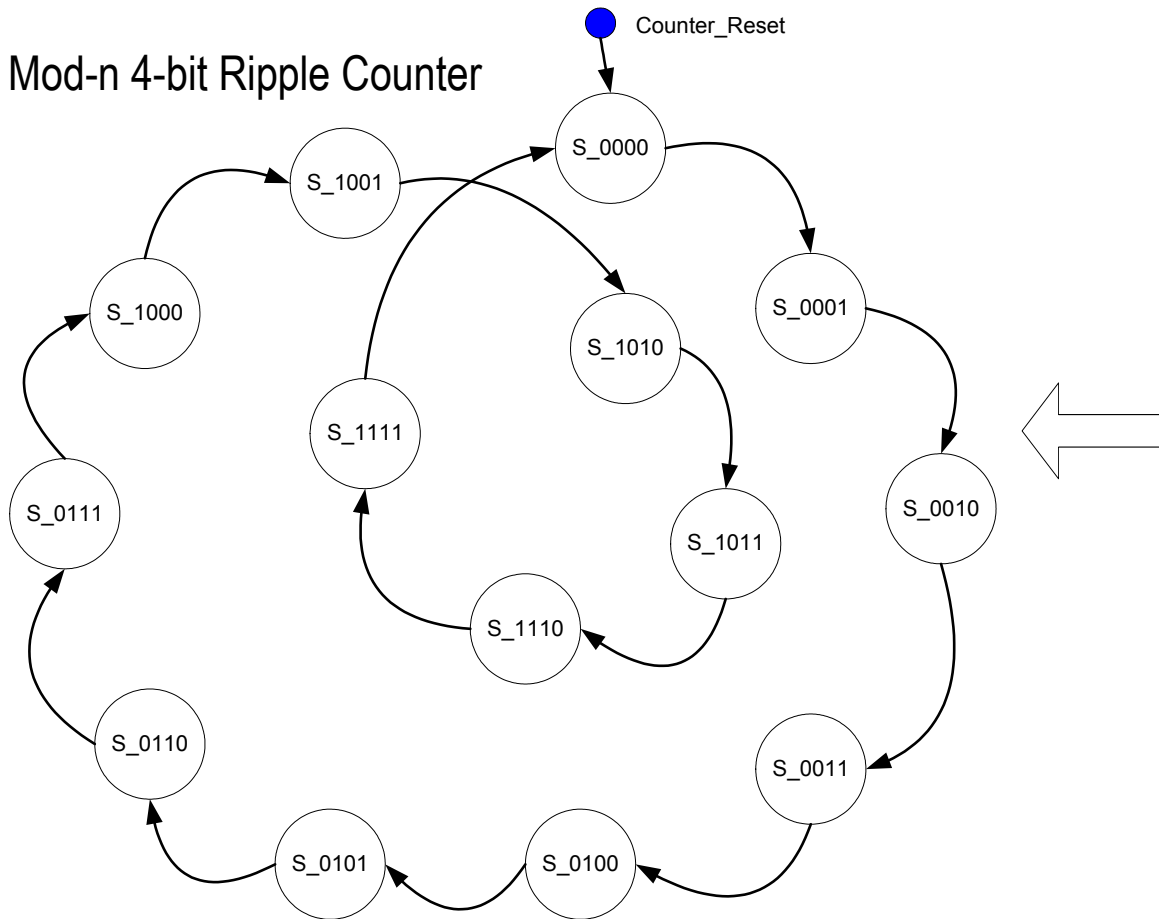


- The second state machine controls the first one. How does it do it?
- How do the transition conditions in Thread 2 affect transitions in Thread 1?

Laboratory ASM Worksheet

Thread_1

 

Thread_2




 


Use this worksheet to hand-draw your initial partitioned ASM design.

Show signal interconnection between the boxes.


Concurrent Mod-n Ripple Counter – Architecture #3

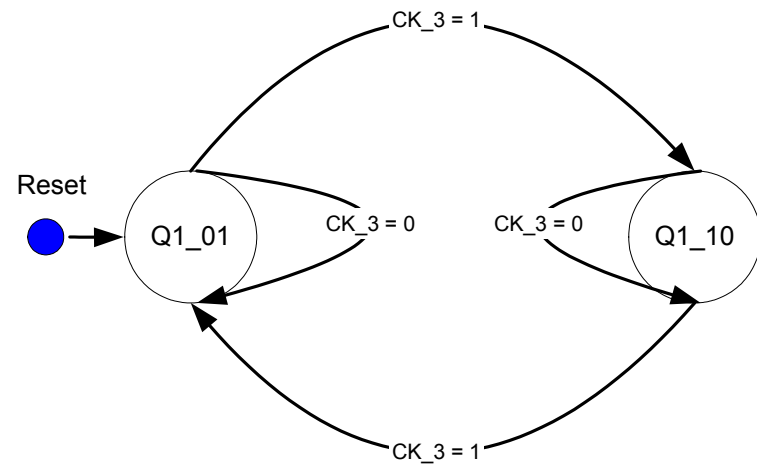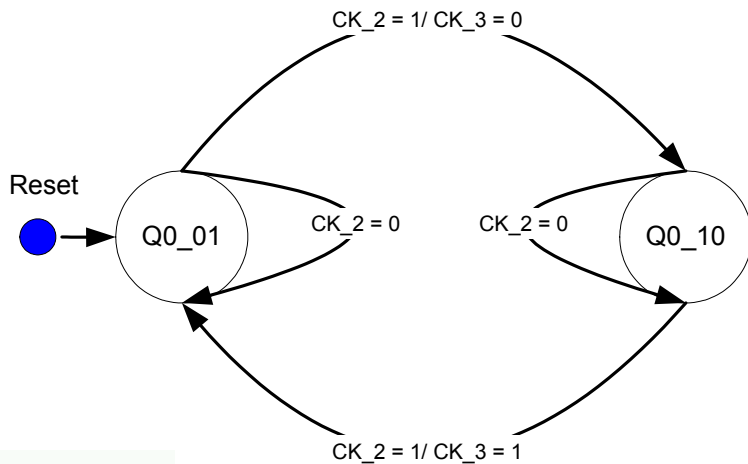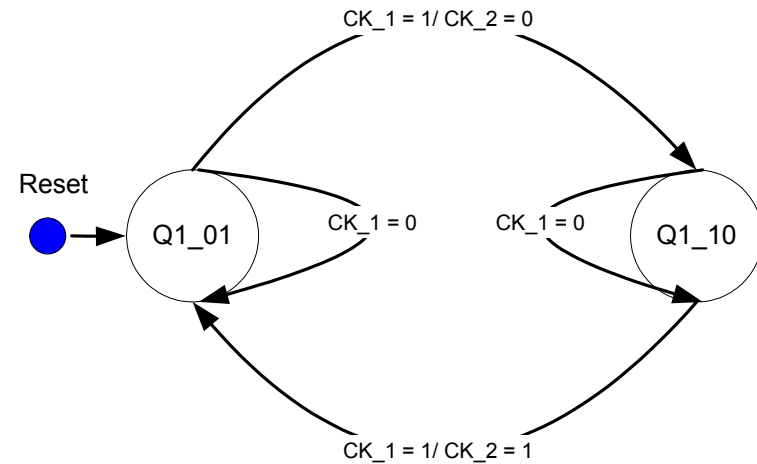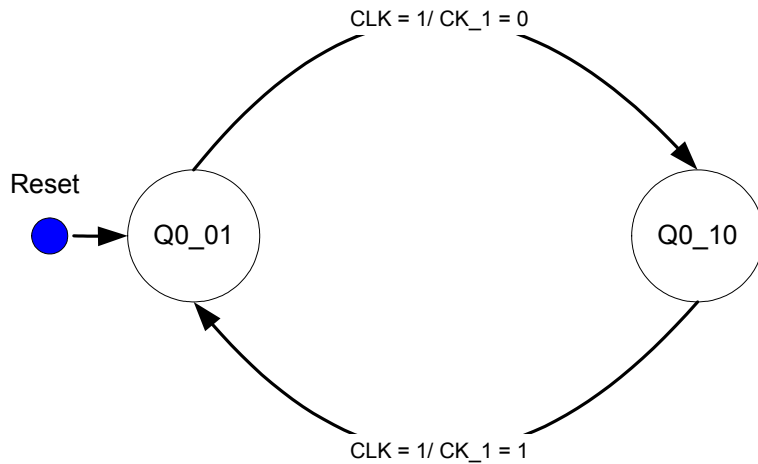- The Nth state machine controls the N+1 one. How does it do it?




Laboratory ASM Worksheet


Thread_1

 


Thread_2

 

Thread_3

 

Thread_4

 

Use this worksheet to hand-draw your initial partitioned ASM design.

Show signal interconnection between the boxes.

Lab Exercise – Modulo Counter Design

- Three architectures – variations on a theme.
 - ✓ Fletcher’s basic Mod-10 4-bit Ripple counter [Fletcher, 1980].
 - ✓ A Mod-n 4-bit programmable Ripple counter – pass in the Mod value as an input, then use a separate control state machine to count to the mod value, then reset the main counter (like Fletcher’s technique, but more flexible).
 - ✓ A concurrent Mod-n 4-bit Ripple counter – have separate state machines for each state register, have one control the clock pulse of the next, which controls the clock of the next, etc. This more clearly shows the “rippling” of the count through the design.
- Lab Assignment.
 - ✓ Create ASM models for each of these Ripple counter architectures in Nimbus. You will need to complete the designs (as these are abstract ideas I am giving you), define the buses, and create the various control structures between the ASM threads. Make sure you have inputs (where required) and counter outputs.
 - ✓ Synthesize each of these in Synopsys® (or other logic synthesis tool, if available).
 - ✓ Turn in output consisting of Nimbus models, Synopsys schematics, and reports.
 - ✓ Remember, if using Synopsys: (1) select class.db as library, (2) Read in the file flowhdl_bit.vhdl, (3) Optimize the design once you’ve read in your model. Then run report.